

EE-241. Introductory Electronics Laboratory

Lab 7 Handout*

LC circuits, resonance and transformers

Fall 2009

Objectives

At the end of this lab you should know

- Resonance in LC circuits.
- Frequency response of LC circuits and bandpass filtering.
- Transformers and how they can be used to induce voltage into an LC circuit.
- Basic principle of an AM radio.

Theory

Background section in Experiment 8 of Y. Tsvividis *pg.* 62 - 66.

Prelab Problems

Consider an LC circuit as shown in Fig. 1 (page 62) with a switch between capacitor and inductor. Assume the circuit resistance and electromagnetic radiation is negligible. Also the initial charge on the capacitor is Q_{max} . If the switch is closed at time $t = 0$, answer the following questions.

1. Quantitatively explain the variation in energy on capacitor and inductor during equal intervals of time $t = \frac{T}{4}$. Where T is the period of oscillation. *Hint: the oscillations in LC circuit are electromagnetic analog to the mechanical (simple harmonic) oscillations of a block of mass m attached to a spring.*
2. Derive an expression for angular resonance frequency ($\omega_{resonance}$), current in the circuit (I) and charge on the capacitor (Q).
 - (a) How does the charge on the capacitor and current in the circuit vary with time? Draw their waveforms. Clearly show the peak values of the two quantities.

*LUMS School of Science & Engineering, Lahore, Pakistan.

- (b) Show that current is 90 degrees out of phase with the charge and the amplitudes of energy stored in inductor and capacitor are equal.
- (c) Note that at some instances of time, the charge on the capacitor is zero but at such instances of time the current is not zero. How is it possible?

Hint: you can start by considering charge on the capacitor and current in the circuit at arbitrary point in time when $Q < Q_{max}$ and $I < I_{max}$. Also note that at any point in time, the total energy stored in the circuit is equal to total initial energy stored in the capacitor at time $t < 0$. Moreover, total energy in the system is always conserved.

- 3. Derive an expression for the total energy in an LC circuit. Show that it is equal to the initial energy stored in the capacitor before time $t = 0$. *Hint: note that the max energy stored in the inductor (when $Q = 0$) is equal to the initial energy stored in the capacitor (when $I = 0$).*

Now let us make our circuit more realistic by adding a resistance R (representing a finite resistance in the LC circuit) in series with the inductor and capacitor. This is called a RLC circuit (analogous to damped oscillator). Assuming the electromagnetic radiation in the circuit is still negligible and the capacitor is initially charged to Q_{max} . If the switch is closed at time $t = 0$, answer the following questions.

- 4. Derive an expression for charge in a RLC circuit. Draw its waveform.
- 5. Give the condition for under-damped, critically-damped and over-damped oscillations in the system. How can you tell when a RLC circuit is overdamped or underdamped? What is the significance of critical damping in RLC circuit?
- 6. Show how charge varies with time in an over-damped RLC circuit. Show peak values of the waveform.